



# Ch12.3 Logic Gates (Week 10)

## Introduction

### Gates

- The basic element of circuits

### Combinational circuits or gating networks

- Circuits that depends only on the input, not on the current state of the circuit
- No memory capabilities

## Basic Types of Gates

### Inverter

- produces the complement



Inverter

### OR gate

- produces sum of the values



OR gate

### AND gate

- produces product of the values




AND gate


## Combinations of Gates
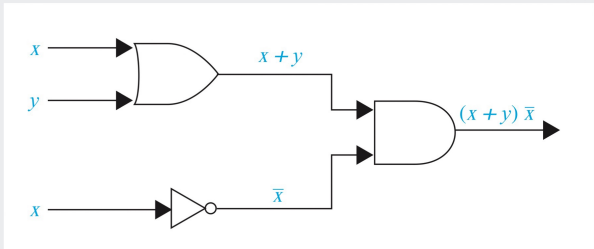
### ▼ Example 1


Construct circuits that produce (a)  $(x + y) \bar{x}$  (b)  $\bar{x} \overline{(y + \bar{z})}$  (c)  $(x + y + z)(\bar{x} \bar{y} \bar{z})$ .



(a)  $(x + y) \bar{x}$

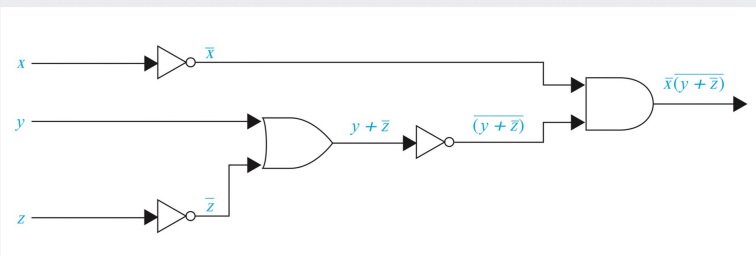

(b)  $\bar{x} \overline{(y + \bar{z})}$

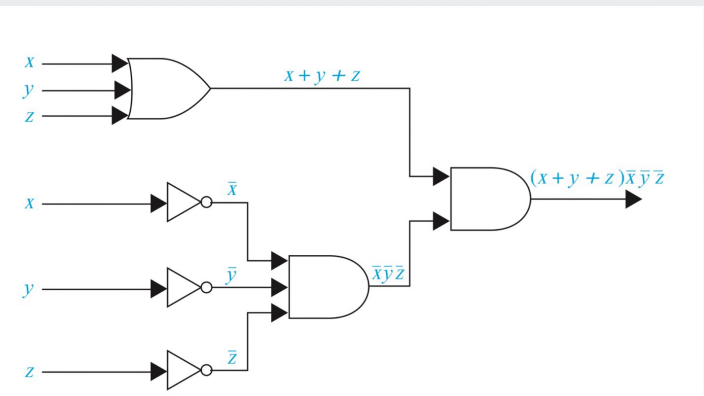


(c)  $(x + y + z)(\bar{x} \bar{y} \bar{z})$

## Examples of Circuits
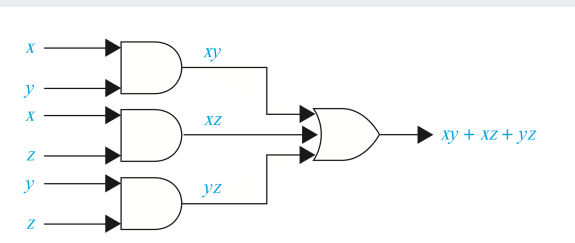
### ▼ Example 2

A total of three individuals are voting for an organization, a proposal passed if it receives at least two yes votes. Design a circuit that determines whether a proposal passes.




A Circuit for Majority Voting

▼ Example 3

Design circuits that switching any of the switches turns the light on when it is off and vice versa when there are two and three switches.


$x = 0$  is open,  $x = 1$  is closed (same for  $y$ ),  $F(x, y) = 1$  light on,  $F(x, y) = 0$  light off.

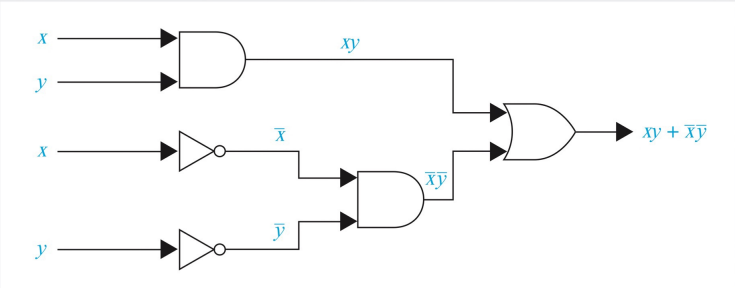Arbitrarily decide that  $F(1, 1) = 1$ , and all other values are determined.



A Circuit for a Light Controlled by Two Switches

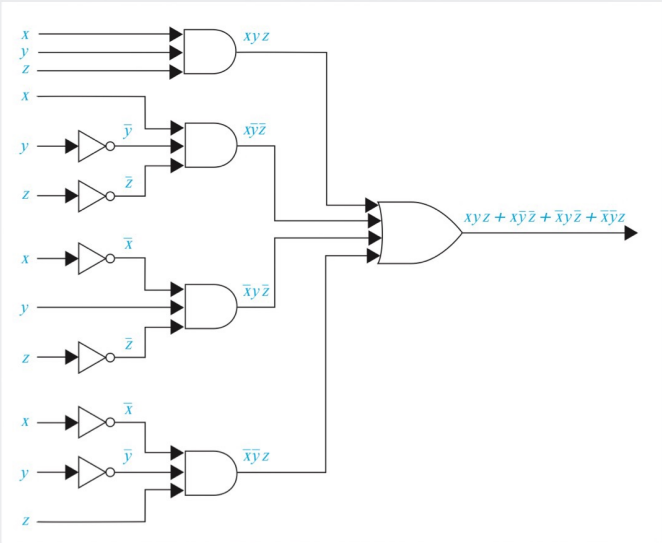Arbitrarily decide that  $F(1, 1, 1) = 1$ , and all other values are determined.



A Circuit for a Fixture Controlled by Three Switches


Adders

Multiple output circuit


- $s$  is the sum bit
- $c$  is the carry bit

Input		Output	
$x$	$y$	$s$	$c$
1	1	0	1
1	0	1	0
0	1	1	0
0	0	0	0


Input and Output for the Half Adder

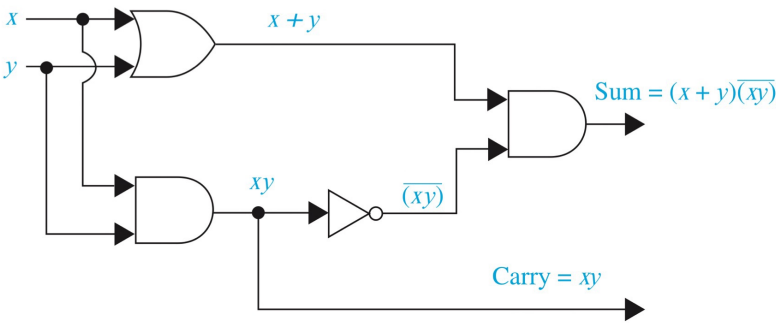

Half Adder

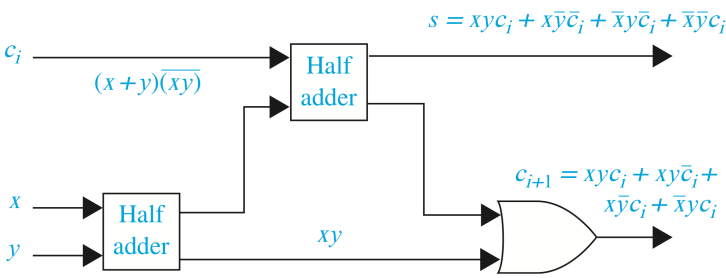

Full Adder

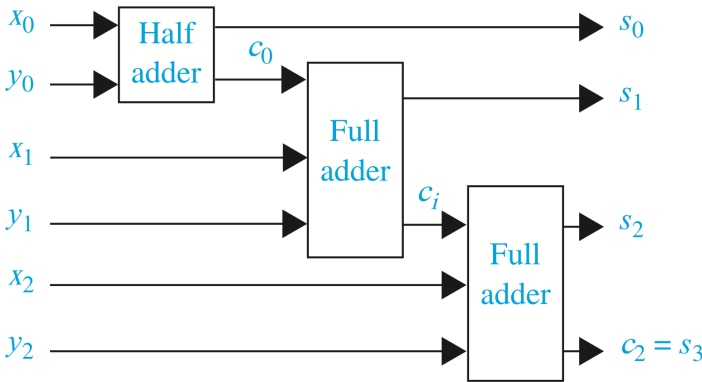

Adding 2 Three-Bit integers with Full and Half Adders