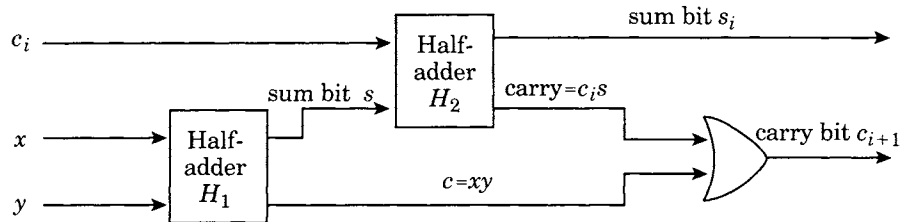


Figure 12.32

A full-adder.



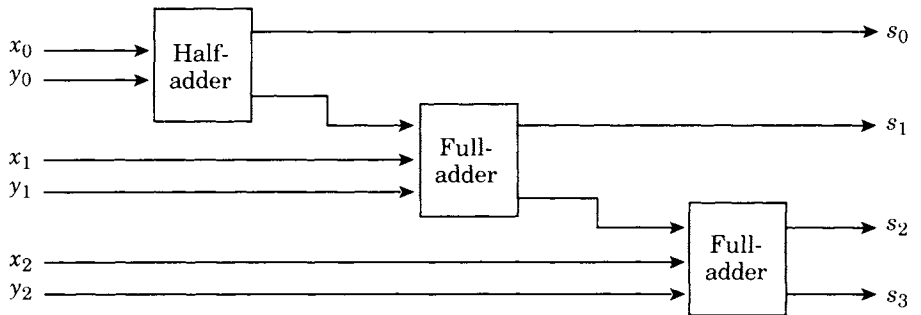
We close this section by showing how we can use half- and full-adders to compute the sum of two n -bit numbers.

EXAMPLE 12.26

Using a half-adder and full-adder, design a circuit that computes the sum of two 3-bit numbers $x = x_2x_1x_0$ and $y = y_2y_1y_0$.

SOLUTION:

A half-adder accepts two bits outputting the sum and carry bits. On the other hand, a full-adder accepts three bits to produce the sum and carry bits. The circuit in Figure 12.33 produces the sum $s = s_3s_2s_1s_0$.

Figure 12.33

The range of possible combinatorial circuits expands as logic gates from half- and full-adders describe many electrical systems through the production of bit sums.

11/18 03:05 do
03:12 correct end
03:13 (wk 10) ↓ more

Exercises 12.4


When will the combinatorial circuit for each boolean expression produce 1 as the output?







1. x' $x=0$ ✓




2. $x + y$ $x=1$ or $y=1$

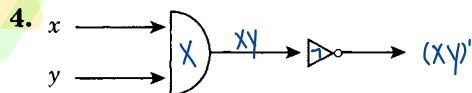3. xy $x=y=1$ ✓

Find the output produced by the combinatorial circuits in Exercises 4–13.



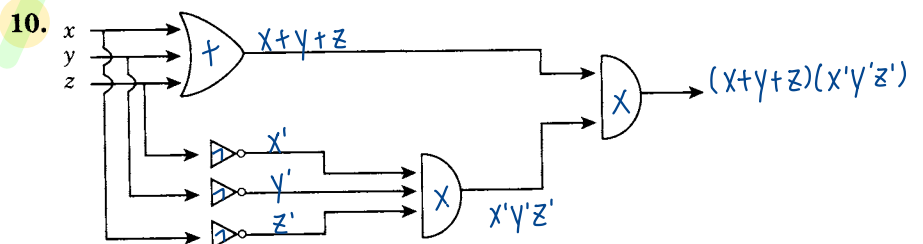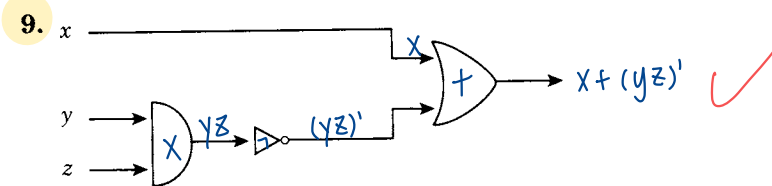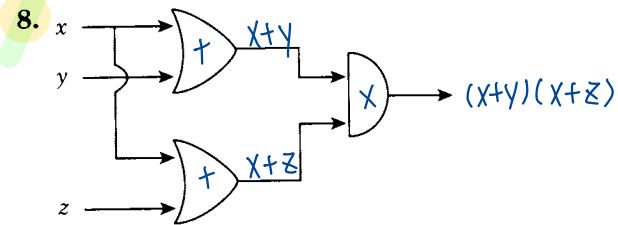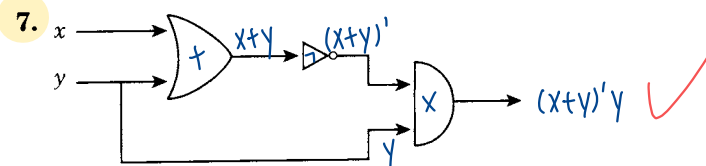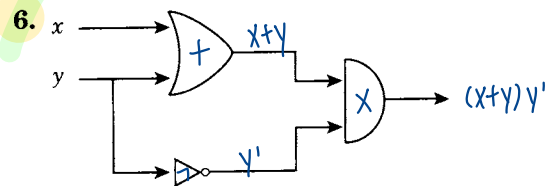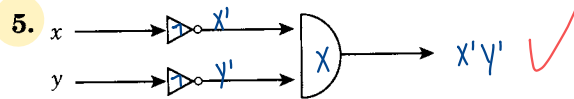

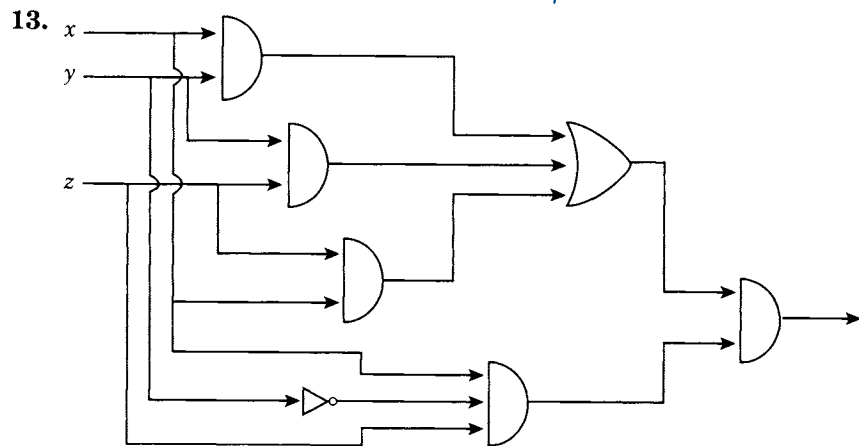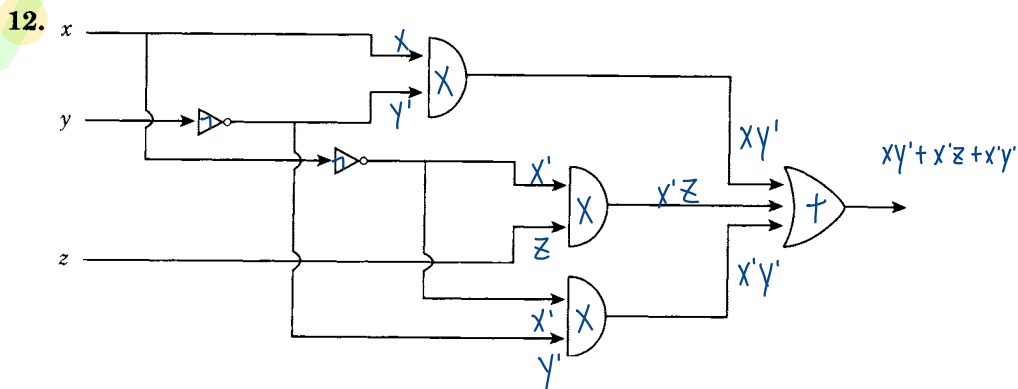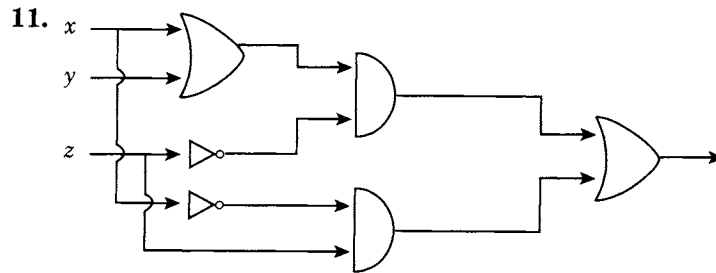

14–17. Devise a logic table for each circuit in Exercises 6–9.

18–21. Construct a combinatorial circuit for each boolean expression in Exercises 9, 10, 14, and 15 in Section 12.2.

Using only NAND gates, design a combinatorial circuit that receives x and y as input signals and outputs:

22. x'

23. $x + y$

24. xy

25–27. Redo Exercises 22–24, using only NOR gates.

Figure 12.44

	yz	yz'	$y'z'$	$y'z$
wx			1	
wx'			1	1
$w'x'$	1	1		
$w'x$	1	1		

(2) Using the Karnaugh map in Figure 12.44, we have:

$$\begin{aligned}
 E_2 &= (wxy'z' + wx'y'z') + (wx'y'z' + wx'y'z) \\
 &\quad + (w'x'yz + w'x'y'z' + w'xyz + w'xy'z') \\
 &= wy'z'(x + x') + wx'y'(z + z') + [w'x'y(z + z') + w'xy(z + z')] \\
 &= wy'z' + wx'y' + (w'x'y + w'xy) \\
 &= wy'z' + wx'y' + w'y(x + x') \\
 &= wy'z' + wx'y' + w'y
 \end{aligned}$$

■

These cases suggest that Karnaugh maps simplify boolean expressions more easily than algebraic laws, especially when variables are few.

11/18 02:48 - 03:00
- correct 03:04 end (Wk10)

Exercises 12.5

	$y'z$	$y'z'$	yz'	yz
x				
x'	1	1	1	1

→ x'

Simplify each boolean expression using the laws of boolean algebra.

- $xy + xy' = x$ ✓
- $x(x + y) + xy' = x$ ✓
- $(x + y)xy' = xy'$ ✓
- $xy + xy' + x'y' = x + y'$ ✓
- $x'yz + x'y'z' + x'yz' + x'y'z = x'$ ✓
- $xy'z' + x'y'z' + xy'z + x'y'z$
- $(x + y)(x + y + z)xy$
- $(x + y + z)xyz$
- $(x + y)(y + z)(z + x)$
- $(xy + yz + zx)xyz$
- $(x + y)(x' + y)(x + y')$
- $(x + y' + z)(x + y + z')xy'z'$
- $(x + y)(y + z)(z + x)xyz$
- $(x + yz)(y + zx)(z + xy)$
- $wxyz + w'xy'z' + wxyz' + w'xy'z$
- $wx'yz + wx'y'z' + w'x'yz' + w'xyz'$

Find the boolean expression represented by each Karnaugh map.

- | | | |
|------|-----|------|
| | y | y' |
| x | 1 | 1 |
| x' | | |
- | | | |
|------|-----|------|
| | y | y' |
| x | 1 | |
| x' | 1 | |
- | | | |
|------|-----|------|
| | y | y' |
| x | | 1 |
| x' | 1 | |
- | | | |
|------|-----|------|
| | y | y' |
| x | 1 | |
| x' | | 1 |

Display each sum of minterms in a Karnaugh map.

- $xy + x'y'$
- $x'y + xy'$

Using a Karnaugh map, simplify each sum of minterms.

not simplifying.

23. $xy + xy'$

24. $xy + xy' + x'y'$

Find the boolean expression represented by each Karnaugh map.

25. $\begin{array}{c|cccc} & yz & yz' & y'z' & y'z \\ \hline x & 1 & 1 & 1 & \\ x' & & & 1 & \end{array} \rightarrow xy + xy' + x'y'z'$

26. $\begin{array}{c|cccc} & yz & yz' & y'z' & y'z \\ \hline x & 1 & & & \\ x' & 1 & 1 & 1 & \end{array} \rightarrow yz + x'z'$

27. $\begin{array}{c|cccc} & yz & yz' & y'z' & y'z \\ \hline x & & 1 & 1 & \\ x' & & 1 & 1 & \end{array} \rightarrow xy + x'y + x'y'z'$

28. $\begin{array}{c|cccc} & yz & yz' & y'z' & y'z \\ \hline x & 1 & & & \\ x' & 1 & 1 & & \end{array} \rightarrow yz + x'y$

29. $\begin{array}{c|cccc} & yz & yz' & y'z' & y'z \\ \hline x & & & 1 & 1 \\ x' & & & & \end{array} \rightarrow xy'$

30. $\begin{array}{c|cccc} & yz & yz' & y'z' & y'z \\ \hline x & & & 1 & 1 \\ x' & & & 1 & 1 \end{array} \rightarrow y'$

Using a Karnaugh map, simplify each boolean expression.

29. $xy'z + xy'z' = xy'$ ✓

30. $xyz + xy'z + x'yz + x'y'z$

31. $xy'z' + xy'z + x'y'z' + x'y'z = y'$ ✓

32. $xyz + xyz' + x'y'z' + x'y'z$

33–36. Using a Karnaugh map, simplify the boolean expressions in Exercises 25–28.

Find the boolean expression represented by each Karnaugh map.

37. $\begin{array}{c|cccc} & yz & yz' & y'z' & y'z \\ \hline wx & & 1 & 1 & \\ wx' & & 1 & 1 & \\ w'x' & & 1 & 1 & \\ w'x & & 1 & 1 & \end{array}$

38. $\begin{array}{c|cccc} & yz & yz' & y'z' & y'z \\ \hline wx & 1 & & & 1 \\ wx' & & & & \\ w'x' & & & & \\ w'x & 1 & & & 1 \end{array}$

39. $\begin{array}{c|cccc} & yz & yz' & y'z' & y'z \\ \hline wx & 1 & & & \\ wx' & 1 & & & \\ w'x' & & & 1 & 1 \\ w'x & & & 1 & 1 \end{array}$

40. $\begin{array}{c|cccc} & yz & yz' & y'z' & y'z \\ \hline wx & 1 & 1 & 1 & \\ wx' & & & 1 & 1 \\ w'x' & & & & \\ w'x & 1 & & & \end{array}$

Represent each sum of minterms in a Karnaugh map.

41. $wxy'z + w'xyz$

42. $wxyz + wxy'z + w'xyz + w'xy'z$

43. $wxy'z + wx'y'z + w'xy'z + w'x'y'z$

44. $wx'yz' + wx'y'z' + w'x'yz' + w'x'y'z'$

45–48. Using a Karnaugh map, simplify the boolean expressions in Exercises 37–40.

Using a Karnaugh map, simplify each boolean expression.

49. $wxyz + wx'yz + w'x'yz + w'xyz$

50. $wx'yz' + wx'y'z' + w'x'yz' + w'x'y'z'$

51. $wx'yz + wx'y'z + w'x'yz + w'x'y'z$

52. $wxyz + wxy'z + wxy'z' + wxy'z + wx'y'z + w'x'y'z + w'x'y'z$